

# **Spartan6 DSP48A1**

FPGA Flow

**Created by : Yousef Gamal**

## Table of Contents

<b>1.</b>	<b>Spartan-6 DSP48A1 Overview .....</b>	<b>3</b>
1.1.	Description .....	3
1.2.	Key Features .....	3
1.3.	Applications.....	3
1.4.	Configuration and Usage .....	3
<b>2.</b>	<b>RTL Code .....</b>	<b>4</b>
2.1.	Pipeline Stage Module .....	4
2.2.	DSP Top Module .....	5
<b>3.</b>	<b>Testbench Code .....</b>	<b>10</b>
<b>4.</b>	<b>Do File .....</b>	<b>15</b>
<b>5.</b>	<b>Waveform .....</b>	<b>16</b>
<b>6.</b>	<b>Transcript .....</b>	<b>16</b>
<b>7.</b>	<b>Constraints.....</b>	<b>17</b>
<b>8.</b>	<b>Elaboration .....</b>	<b>17</b>
8.1.	Messages tab .....	17
8.2.	Schematic .....	18
<b>9.</b>	<b>Synthesis.....</b>	<b>19</b>
9.1.	Messages tab .....	19
9.1.1.	Comments on Warnings.....	19
9.2.	Netlist Generation .....	20
9.3.	Report timing summary .....	21
9.4.	Utilization Report .....	21
<b>10.</b>	<b>Implementation .....</b>	<b>21</b>
10.1.	Message tab .....	21
10.2.	Device.....	22
10.3.	Design timing summary .....	22
10.4.	Utilization Report.....	23
10.4.1.	Hierarchy.....	23
10.4.2.	Summary.....	23



## 2. RTL Code

### 2.1. Pipeline Stage Module

```
module pipeline_stage #(
    parameter WIDTH = 8,
    parameter reset_type = "ASYNC",
    parameter sel = 1 )
(
    input [WIDTH-1:0] DATA_IN,
    input CLK,
    input reset,
    input ENABLE,
    output reg [WIDTH-1:0] DATA_OUT
);

generate
    if (sel)
        begin
            // Registering Data
            if (reset_type == "SYNC")
                begin
                    always @(posedge CLK)
                    begin
                        if (reset)
                            DATA_OUT <= {WIDTH{1'b0}};
                        else if (ENABLE)
                            DATA_OUT <= DATA_IN;
                    end
                end
            else if (reset_type == "ASYNC")
                begin
                    always @(posedge CLK or posedge reset)
                    begin
                        if (reset)
                            DATA_OUT <= {WIDTH{1'b0}};
                        else if (ENABLE)
                            DATA_OUT <= DATA_IN;
                    end
                end
            end
        end
    else
        begin
            // Bypassing Data
            always @(*)
            begin
                DATA_OUT = DATA_IN;
            end
        end
    end
endgenerate
endmodule
```

## 2.2. DSP Top Module

```
module DSP_top_module
#(
    /*-----specify the number of pipeline registers for input paths.-----*/

    parameter A0REG      = 0 , /* no register */
    parameter A1REG      = 1 , /* one register */
    parameter B0REG      = 0 , /* no register */
    parameter B1REG      = 1 , /* one register */
    parameter CREG       = 1 , /* one register */
    parameter DREG       = 1 , /* one register */
    parameter MREG       = 1 , /* one register */
    parameter PREG       = 1 , /* one register */
    parameter CARRYINREG = 1 , /* one register */
    parameter CARRYOUTREG = 1 , /* one register */
    parameter OPMODEREG  = 1 , /* one register */

    /*---determine the carry cascade input source, Values CARRYIN or opcode[5].---*/
    /*---If neither "CARRYIN" nor "OPMODE5" is set, the output is tied to 0.---*/
    parameter CARRYINSEL = "OPMODE5" , /* default value */

    /*---specifies the source of the input to the B port-----*/
    /*---DIRECT: The B port gets its input directly from the B input of the slice.---*/
    /*---CASCADE: The B port gets its input from the BCIN (B cascaded input) of the
        previous DSP48A1 slice.--*/
    /*----- else ==> the mux output should be Zero -----*/
    parameter B_INPUT = "DIRECT" ,

    /*--determines the reset for the DSP48A1 slice is synchronous or asynchronous--*/
    /*--ASYNC: Resets occur asynchronously----- */
    /*--SYNC : Resets occur synchronously-----*/
    parameter RSTTYPE = "SYNC" ,

    /*parameters for cascading DSP48A1*/
    parameter BCIN_val = 18'd2024
)
(
    /*-----input and output ports-----*/

    input CLK , /*--DSP clock--*/
    input [7: 0]OPMODE ,
    /*--Control input to select the arithmetic operations of the DSP48A1 slice--*/

    input [17:0] A ,
    /* input to multiplier && optionally to post_adder/subtractor depending on OPMODE[1:0].*/

    input [17:0] B , /* pre-adder/subtractor input/ multiplier based on OPMODE[4]/ post-
        adder/subtractor based on OPMODE[1:0].*/

```

```

input [17:0] D ,
/* pre-adder/subtractor input | D[11:0] are concatenated with A and B and optionally */
/*sent to post-adder/subtractor depending on the value of OPMODE[1:0]. */

input [47:0] C , /* input to post-adder/subtractor*/
input CARRYIN , /* carry input to the post-adder/subtractor*/

input CEA , /*Clock enable for the A port registers (A0REG & A1REG)*/
input CEB , /*Clock enable for the B port registers (B0REG & B1REG)*/
input CEC , /*Clock enable for the C port registers (CREG) */
input CED , /*Clock enable for the D port registers (DREG) */
input CEM , /*Clock enable for the multiplier registers (MREG). */
input CEP , /*Clock enable for the P output port registers: (PREG = 1). */
input CEOPMODE , /*Clock enable for the opmode register (OPMODEREG).*/
input CECARRY_IN_OUT ,
/*Clock enables the carry-in register and the carry-out register.*/

/*--All resets are active high. sync or async depending on the parameter RSTTYPE--*/

input RSTA , /*Reset for the A registers: (A0REG & A1REG).*/
input RSTB , /*Reset for the B registers: (B0REG & B1REG).*/
input RSTC , /*Reset for the C registers: (CREG).*/
input RSTCARRY_IN_OUT , /*Reset for the carry-in register and the carry-out register*/
input RSTD , /*Reset for the D register (DREG)*/
input RSTM , /*Reset for the multiplier register (MREG)*/
input RSTOPMODE , /*Reset for the opmode register (OPMODEREG).*/
input RSTP , /*Reset for the P output registers (PREG = 1).*/

input [47:0] PCIN , /*Cascade input for Port P.*/
input [17:0] BCIN , /*Cascade input for Port B.*/

output [17:0] BCOUT , /*Cascade output for Port B.*/
output [47:0] PCOUT , /*Cascade output for Port P.*/

output [35:0] M , /* buffered multiplier data output*/
/* MREG = 1 ==> output of multiplier is registered */
/* MREG = 0 ==> Direct output of multiplier */

output [47:0] P , /*output of post adder/subtractor */
/* PREG = 1 ==> output is registered */
/* PREG = 0 ==> Direct output */

output CARRYOUT, /*carry out signal from post adder / subtractor */
/* CARRYOUTREG = 1 ==> output is registered */
/* CARRYOUTREG = 0 ==> Direct output */

output CARRYOUTF /*It is a copy of the CARRYOUT signal */

);

```

```

/*-----instantiate the pipelines stages-----*/
/*-----parameters(WIDTH , reset_type , sel)-----*/
/*-----inputs(DATA_IN , CLK , reset , ENABLE) -----outputs(DATA_OUT)-----*/

wire signed [17:0] D_stage_out , A0_stage_out , A1_stage_out , B0_stage_out, B1_stage_out;
wire signed [47:0] C_stage_out ;
wire signed [7 :0] OPMODE_stage_out ;

pipeline_stage #(.WIDTH(18) , .reset_type(RSTTYPE) , .sel(DREG) ) D_STAGE
( .DATA_IN(D) , .CLK(CLK) , .reset(RSTD) , .ENABLE(CED) , .DATA_OUT(D_stage_out) ) ;

generate
    if(B_INPUT == "DIRECT")
        begin : direct_case
            pipeline_stage #(.WIDTH(18) , .reset_type(RSTTYPE) , .sel(B0REG) ) B0_STAGE
( .DATA_IN(B) , .CLK(CLK) , .reset(RSTB), .ENABLE(CEB) , .DATA_OUT(B0_stage_out));
            end

            else if (B_INPUT == "CASCADE")
                begin : cascade_case
                    pipeline_stage #(.WIDTH(18) , .reset_type(RSTTYPE) , .sel(B0REG) ) B0_STAGE
( .DATA_IN(BCIN_val), .CLK(CLK), .reset(RSTB), .ENABLE(CEB) , .DATA_OUT(B0_stage_out) ) ;
                    end

                else
                    begin : default_case
                        assign B0_stage_out = 18'h00000;
                    end
endgenerate

pipeline_stage #(.WIDTH(18) , .reset_type(RSTTYPE) , .sel(A0REG) ) A0_STAGE
( .DATA_IN(A) , .CLK(CLK) , .reset(RSTA) , .ENABLE(CEA) , .DATA_OUT(A0_stage_out));

pipeline_stage #(.WIDTH(48) , .reset_type(RSTTYPE) , .sel(CREG) ) C_STAGE
( .DATA_IN(C) , .CLK(CLK) , .reset(RSTC) , .ENABLE(CEC) , .DATA_OUT(C_stage_out));

    pipeline_stage #(.WIDTH(8) , .reset_type(RSTTYPE) , .sel(OPMODEREG) ) OPMODE_STAGE
(.DATA_IN(OPMODE),.CLK(CLK),.reset(RSTOPMODE), .ENABLE(CEOPMODE),
    .DATA_OUT(OPMODE_stage_out) );

reg [17:0] pre_adder_sub_output_stage , B1_stage_in ;

always@(*)
begin
    if(OPMODE_stage_out[6])
        pre_adder_sub_output_stage = D_stage_out - B0_stage_out ;
    else
        pre_adder_sub_output_stage = D_stage_out + B0_stage_out ;

        if( OPMODE_stage_out[4] )
            B1_stage_in = pre_adder_sub_output_stage ;

```

```

        else
            B1_stage_in = B0_stage_out ;

end

    pipeline_stage #(.WIDTH(18) , .reset_type(RSTTYPE) , .sel(B1REG) ) B1_STAGE
    ( .DATA_IN(B1_stage_in) , .CLK(CLK) , .reset(RSTB) , .ENABLE(CEB) ,
.DATA_OUT(B1_stage_out) ) ;

    assign BCOUT = B1_stage_out ;

    pipeline_stage #(.WIDTH(18) , .reset_type(RSTTYPE) , .sel(A1REG) ) A1_STAGE
    ( .DATA_IN(A0_stage_out) , .CLK(CLK) , .reset(RSTA) , .ENABLE(CEA) ,
.DATA_OUT(A1_stage_out) ) ;

wire signed [35:0] mutliplier_stage_out ;

assign mutliplier_stage_out = A1_stage_out * B1_stage_out ;

    pipeline_stage #(.WIDTH(36) , .reset_type(RSTTYPE) , .sel(MREG) ) M_STAGE
    (.DATA_IN(mutliplier_stage_out) , .CLK(CLK), .reset(RSTM), .ENABLE(CEM) ,.DATA_OUT(M));

wire current_carry_in ;

generate

    if(CARRYINSEL == "OPMODE5")
        assign current_carry_in = OPMODE_stage_out[5] ;

    else if(CARRYINSEL == "CARRYIN")
        assign current_carry_in = CARRYIN ;

endgenerate

wire CIN ;

    pipeline_stage #(.WIDTH(1) , .reset_type(RSTTYPE) , .sel(CARRYINREG) ) CYI_STAGE
    ( .DATA_IN(current_carry_in) , .CLK(CLK) , .reset(RSTCARRY_IN_OUT) ,
.ENABLE(CECARRY_IN_OUT) , .DATA_OUT(CIN) ) ;

reg [47:0] Z_mux_stage_out, X_mux_stage_out;
reg [47:0] post_adder_sub_output_stage;
reg [48:0] post_adder_sub_temp ;
reg CY0_in;

```



```

always@(*)
begin
    case( {OPMODE_stage_out[3] , OPMODE_stage_out[2] } )

        2'b00: Z_mux_stage_out = 48'h000000000000 ;
        2'b01: Z_mux_stage_out = PCIN ;
        2'b10: Z_mux_stage_out = P ;
        2'b11: Z_mux_stage_out = C_stage_out ;

    endcase

    case( {OPMODE_stage_out[1] , OPMODE_stage_out[0] } )

        2'b00: X_mux_stage_out = 48'h000000000000 ;
        2'b01: X_mux_stage_out = { { 12{mutliplier_stage_out[35]} } ,
mutliplier_stage_out } ;
        2'b10: X_mux_stage_out = P ;
        2'b11: X_mux_stage_out = { D_stage_out[11:0] , A1_stage_out[17:0]
, B1_stage_out[17:0] } ;

    endcase

    if( OPMODE_stage_out[7] )

        post_adder_sub_temp = Z_mux_stage_out - (X_mux_stage_out + CIN) ;
    else
        post_adder_sub_temp = Z_mux_stage_out + X_mux_stage_out + CIN ;

        post_adder_sub_output_stage = post_adder_sub_temp[47 : 0] ;
        CYO_in = post_adder_sub_temp[48] ;

    end

    pipeline_stage #(.WIDTH(1) , .reset_type(RSTTYPE) , .sel(CARRYOUTREG) ) CYO_STAGE
( .DATA_IN(CYO_in) , .CLK(CLK) , .reset(RSTCARRY_IN_OUT) , .ENABLE(CECARRY_IN_OUT) ,
.DATA_OUT(CARRYOUT) ) ;

    assign CARRYOUTF = CARRYOUT ;

    pipeline_stage #(.WIDTH(48) , .reset_type(RSTTYPE) , .sel(PREG) ) P_STAGE
( .DATA_IN(post_adder_sub_output_stage) , .CLK(CLK) , .reset(RSTP) , .ENABLE(CEP) ,
.DATA_OUT(P) ) ;

    assign PCOUT = P ;

endmodule

```

### 3. Testbench Code

```
/* This testbench is done for some default value */

/* if we need to change it pass the required paramter to DUT and change the delay */
/* Defaults ==> A0 , B0 are not exist */
/* Defaults ==> carry in is opmode [5] */
/* Defaults ==> disable cascading for port B*/
/* Defaults ==> synchronous reset*/

module DSP_tb ;

    reg CLK ;
    reg [7: 0]OPMODE ;
    reg [17:0] A , B , D ;
    reg [17:0] BCIN ;
    reg [47:0] PCIN ;
    reg [47:0] C ;
    reg CARRYIN ;
    reg CEA ,CEB , CEC , CED , CEM , CEP ;
    reg CEOPMODE ;
    reg CECARRY_IN_OUT ;
    reg RSTA , RSTB , RSTC , RSTD , RSTM , RSTP ;
    reg RSTCARRY_IN_OUT ;
    reg RSTOPMODE ;

    wire [17:0]BCOUT ;
    wire [47:0]PCOUT ;
    wire [35:0] M ;
    wire [47:0] P ;
    wire CARRYOUT ;
    wire CARRYOUTF ;

    reg [17:0]BCOUT_expected ;
    reg [47:0]PCOUT_expected ;
    reg [35:0] M_expected ;
    reg [47:0] P_expected ;
    reg CARRYOUT_expected ;
    reg CARRYOUTF_expected ;

    DSP_top_module DUT (.*) ;

    always
    begin
        CLK = 0 ;
        #10 ;
        CLK = 1 ;
        #10 ;
    end
```

```

initial
begin
    $display("          start simulation :) ");
    $display(" ===== ");

    /*-----initialize Data ports to Zero at -Ve edge Clock -----*/
@ (negedge CLK) ;
A = 0 ; B = 0 ; D = 0 ; C = 0;
CEA = 0; CEB = 0; CEC = 0;
CED = 0; CEM = 0; CEP = 0;
RSTOPMODE = 0; RSTCARRY_IN_OUT = 0;
CARRYIN = 0; OPMODE = 0;
CEOPMODE = 0; CECARRY_IN_OUT = 0;
RSTA = 0; RSTB = 0; RSTC = 0;
RSTD = 0; RSTM = 0; RSTP = 0;
BCIN = 0; PCIN = 0;

repeat(2)@ (negedge CLK) ; // hold the data for 2 clock cycles

    /* Check the reset functionality */
    /* Initialize reset by 1*/
        RSTA = 1; RSTB = 1; RSTC = 1;
        RSTD = 1; RSTM = 1; RSTP = 1;
        RSTOPMODE = 1; RSTCARRY_IN_OUT = 1;

    /* -----Expect the all output signals to be Zero----- */

BCOUT_expected = 18'h00000 ;    PCOUT_expected = 48'h000000000000 ;
M_expected = 36'h000000000 ;    P_expected = 48'h000000000000 ;
CARRYOUT_expected = 1'b0 ;    CARRYOUTF_expected = 1'b0 ;

    @ (negedge CLK); // synchronous the outputs with -Ve edge Clock

if (
    BCOUT_expected != BCOUT || PCOUT_expected != PCOUT || M_expected != M_expected ||
    P_expected != P || CARRYOUT_expected != CARRYOUT || CARRYOUTF_expected != CARRYOUTF
)
begin
    $display("Error for reset at time : %t" , $time);
end

    /*-----checking for adders/subtractors and multiplier using direct cases-----*/
    /*-----Disable the reset -----*/
    /*-----Direct case one add / add-----*/

@ (negedge CLK) ; // stimulate at -Ve edge Clock

RSTA = 0; RSTB = 0; RSTC = 0;
RSTD = 0; RSTM = 0; RSTP = 0;
RSTOPMODE = 0; RSTCARRY_IN_OUT = 0;

CEA = 1 ; CEB = 1 ; CEC = 1 ;
CEM = 1 ; CEP = 1 ; CED = 1 ;

```

```

CEOPMODE = 1 ; CECARRY_IN_OUT = 1 ;

D = 18'd10 ; B = 18'd20 ; A = 18'd40 ; OPMODE[6] = 0 ; OPMODE[4] = 1 ;
// addition and pass the value (30) to multiplier which pass the value( 40*(10+20) )
M_expected = 1200 ; BCOUT_expected = 30 ;
OPMODE[1:0] = 2'b01 ; // pass the value (1200)
OPMODE[3:2] = 2'b00 ; // add Zero with the value 1200
OPMODE[7] = 0 ; // addition op
OPMODE[5] = 1 ; // carry in ==> the addition will be 1201
P_expected = 48'd1201 ; PCOUT_expected = 1201;
CARRYOUT_expected = 0 ;
CARRYOUTF_expected = 0 ;

repeat(4)@(negedge CLK) ; // synchronous the output with delay of registers

if (
    BCOUT_expected != BCOUT || PCOUT_expected != PCOUT || M_expected != M_expected ||
    P_expected != P || CARRYOUT_expected != CARRYOUT || CARRYOUTF_expected != CARRYOUTF
)
    begin
        $display("Error for arithmetic operations at time : %t" , $time);
    end
/*----- Direct case two pass then add -----*/

@(negedge CLK) ; // stimulate at -Ve edge Clock

B = 18'd46 ; A = 18'd10 ; OPMODE[4] = 0 ;
// pass the value (46) to multiplier which passes the value( 10*(46) )
M_expected = 460 ; BCOUT_expected = 46 ;
OPMODE[1:0] = 2'b01 ; // pass the value (460)
OPMODE[3:2] = 2'b00 ; // add Zero with the value 460
OPMODE[7] = 0 ; // add op
OPMODE[5] = 1 ; // carry in ==> the subtraction will be 461

P_expected = 48'd461 ; PCOUT_expected = 48'd461;
CARRYOUT_expected = 0 ;
CARRYOUTF_expected = 0 ;

repeat(4)@(negedge CLK) ; // synchronous the output with delay of registers

if (
    BCOUT_expected != BCOUT || PCOUT_expected != PCOUT || M_expected != M_expected ||
    P_expected != P || CARRYOUT_expected != CARRYOUT || CARRYOUTF_expected != CARRYOUTF
)
    begin
        $display("Error for arithmetic operations at time : %t" , $time);
    end
end

```

```

/*----- Direct case three sub then add -----*/

@(negedge CLK) ; // stimulate at -Ve edge Clock

D = 18'd50 ; B = 18'd35 ; A = 18'd10 ; OPMODE[4] = 1 ; OPMODE[6] = 1 ;
// pass the value (15) to multiplier which passes the value( 10*(50-35) )
M_expected = 150 ; BCOUT_expected = 15 ;
OPMODE[1:0] = 2'b01 ; // pass the value (150)
OPMODE[3:2] = 2'b00 ; // add Zero with the value 150
OPMODE[7] = 0 ; // add op
OPMODE[5] = 1 ; // carry in ==> the subtraction will be 151

P_expected = 48'd151 ; PCOUT_expected = 48'd151;
CARRYOUT_expected = 0 ;
CARRYOUTF_expected = 0 ;

repeat(4)@(negedge CLK) ; // synchronous the output with delay of registers

if (
    BCOUT_expected != BCOUT || PCOUT_expected != PCOUT || M_expected != M_expected ||
    P_expected != P || CARRYOUT_expected != CARRYOUT || CARRYOUTF_expected != CARRYOUTF
)
    begin
        $display("Error for arithmetic operations at time : %t" , $time);
    end

/*----- Direct case Four sub / add -----*/

@(negedge CLK); // stimulate at -Ve edge Clock

D = 18'd1000 ; B = 18'd200 ; A = 18'd4 ; OPMODE[6] = 1 ; OPMODE[4] = 1 ;
// subtraction and pass the value (800) to multiplier which pass the value( 4*(1000 - 200) )
M_expected = 3200 ; BCOUT_expected = 800 ;
OPMODE[1:0] = 2'b01 ; // pass the value (3200)
C = 48'd1200;
OPMODE[3:2] = 2'b11 ; // add C + M + cin
OPMODE[7] = 0 ; // addition op
OPMODE[5] = 1 ; // carry in ==> the subtraction will be 4401

P_expected = 48'd4401 ; PCOUT_expected = 48'd4401 ;
CARRYOUT_expected = 0 ;
CARRYOUTF_expected = 0 ;

repeat(4)@(negedge CLK) ; // synchronous the output with delay of registers

if (
    BCOUT_expected != BCOUT || PCOUT_expected != PCOUT || M_expected != M_expected ||
    P_expected != P || CARRYOUT_expected != CARRYOUT || CARRYOUTF_expected != CARRYOUTF
)
    begin
        $display("Error for arithmetic operations at time : %t" , $time);
    end
end

```

```

/*-----Direct case five sub / sub -----*/

@(negedge CLK); // stimulate at -Ve edge Clock

D = 18'd1000 ; B = 18'd200 ; A = 18'd4 ; OPMODE[6] = 1 ; OPMODE[4] = 1 ;
// subtraction and pass the value (800) to multiplier which pass the value( 4*(1000 - 200)
)
M_expected = 3200 ; BCOUT_expected = 800 ;
OPMODE[1:0] = 2'b01 ; // pass the value (3200)
C = 48'd5600;
OPMODE[3:2] = 2'b11 ; // add C - M - cin
OPMODE[7] = 1 ; // subtraction op
OPMODE[5] = 1 ; // carry in ==> the subtraction will be 4401

P_expected = 48'd2399 ; PCOUT_expected = 48'd2399 ;
CARRYOUT_expected = 0 ;
CARRYOUTF_expected = 0 ;

repeat(4)@(negedge CLK) ; // synchronous the output with delay of registers

if (
    BCOUT_expected != BCOUT || PCOUT_expected != PCOUT || M_expected != M_expected ||
    P_expected != P || CARRYOUT_expected != CARRYOUT || CARRYOUTF_expected != CARRYOUTF
)
    begin
        $display("Error for arithmetic operations at time : %t" , $time);
    end

/*-----Last Direct case sub / sub for -Ve numbers -----*/

@(negedge CLK); // stimulate at -Ve edge Clock

D = -18'd500 ; B = 18'd200 ; A = 18'd5 ; OPMODE[6] = 1 ; OPMODE[4] = 1 ;
// subtraction and pass the value (-700) to multiplier which pass the value( 5*(-500 -
200) )
M_expected = -3500 ; BCOUT_expected = -700 ;
OPMODE[1:0] = 2'b01 ; // pass the value (-3500)
C = 48'd5600;
OPMODE[3:2] = 2'b11 ; // add C - M - cin
OPMODE[7] = 1 ; // subtraction op
OPMODE[5] = 1 ; // carry in ==> the subtraction will be 4401

P_expected = 48'h00000000238B ; PCOUT_expected = 48'h00000000238B ; // this values for
Sign extension operation
CARRYOUT_expected = 1;
CARRYOUTF_expected = 1 ;

```

```

repeat(4)@(negedge CLK) ; // synchronous the output with delay of registers

if (
    BCOUT_expected != BCOUT || PCOUT_expected != PCOUT || M_expected != M_expected ||
    P_expected != P || CARRYOUT_expected != CARRYOUT || CARRYOUTF_expected != CARRYOUTF
)
    begin
        $display("Error for arithmetic operations at time : %t" , $time);
    end

$display("---- The testbench is done successfully :) -----");
$stop;
end
endmodule

```

## 4. Do File

```

# open work for projects
vlib work

# compile files
vlog DSP_top_module.v DSP_TB.v Pipeline_stage.v

# simulate testbench

vsim -voptargs="+acc" work.DSP_tb


add wave *

# for the DUT internal signals
add wave /DUT/*

# run the simulation
run -all

```

## 5. Waveform

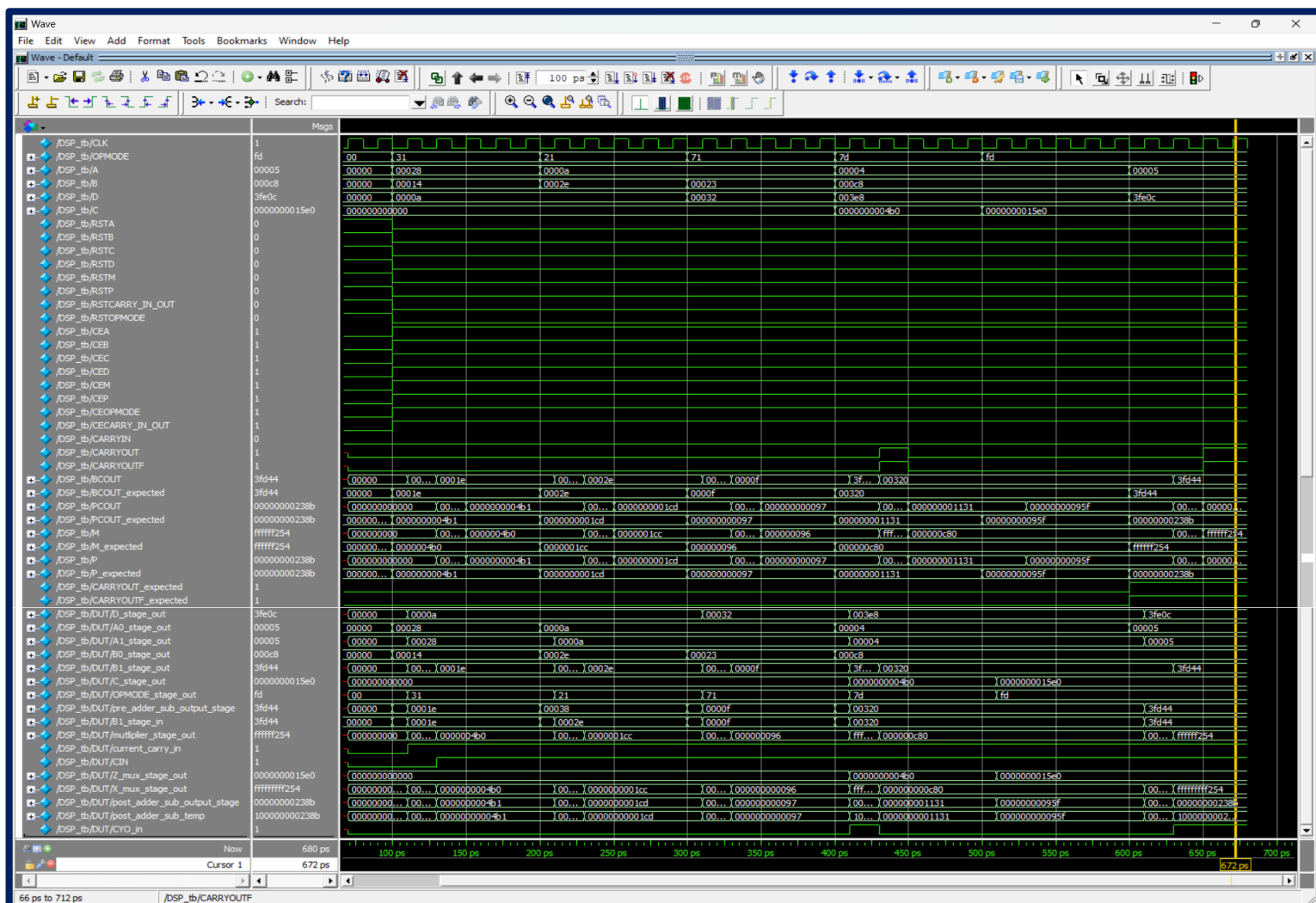

## 6. Transcript

```

Transcript
VSIM 3> run -all
#          start simulation :)
#
# =====
# ---- The testbench is done successfully :) ----
# ** Note: $stop      : DSP_TB.v(267)
#      Time: 680 ps  Iteration: 1  Instance: /DSP_tb
# Break in Module DSP_tb at DSP_TB.v line 267

```



## 7. Constraints


```
## Clock signal
# w5 PIN CONNECTED TO CLOCK 33 IS THE DEFINITION OF 3.3v PASSED TO PINS
set_property -dict {PACKAGE_PIN W5 IOSTANDARD LVCMOS33} [get_ports CLK]
#add the name of clock in design after -name
create_clock -period 10.000 -name CLK -waveform {0.000 5.000} -add [get_ports CLK]

## Configuration options, can be used for all designs
set_property CONFIG_VOLTAGE 3.3 [current_design]
set_property CFGBVS VCC0 [current_design]



## SPI configuration mode options for QSPI boot, can be used for all designs
set_property BITSTREAM.GENERAL.COMPRESS TRUE [current_design]
set_property BITSTREAM.CONFIG.CONFIGRATE 33 [current_design]
set_property CONFIG_MODE SPIx4 [current_design]
```

## 8. Elaboration

## 8.1. Messages tab

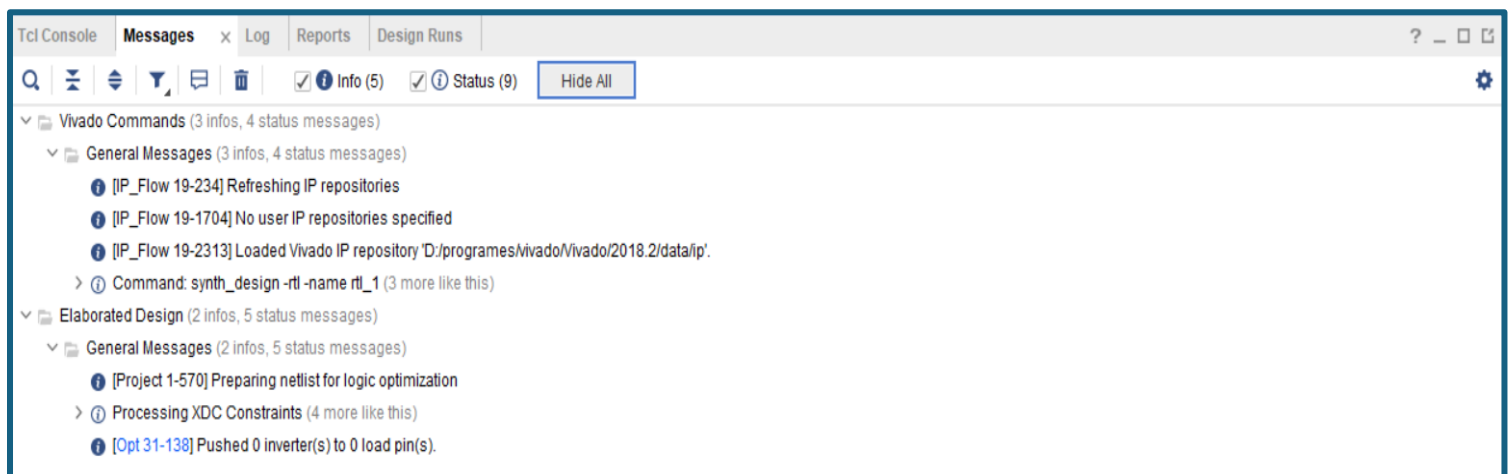


## 8.2. Schematic

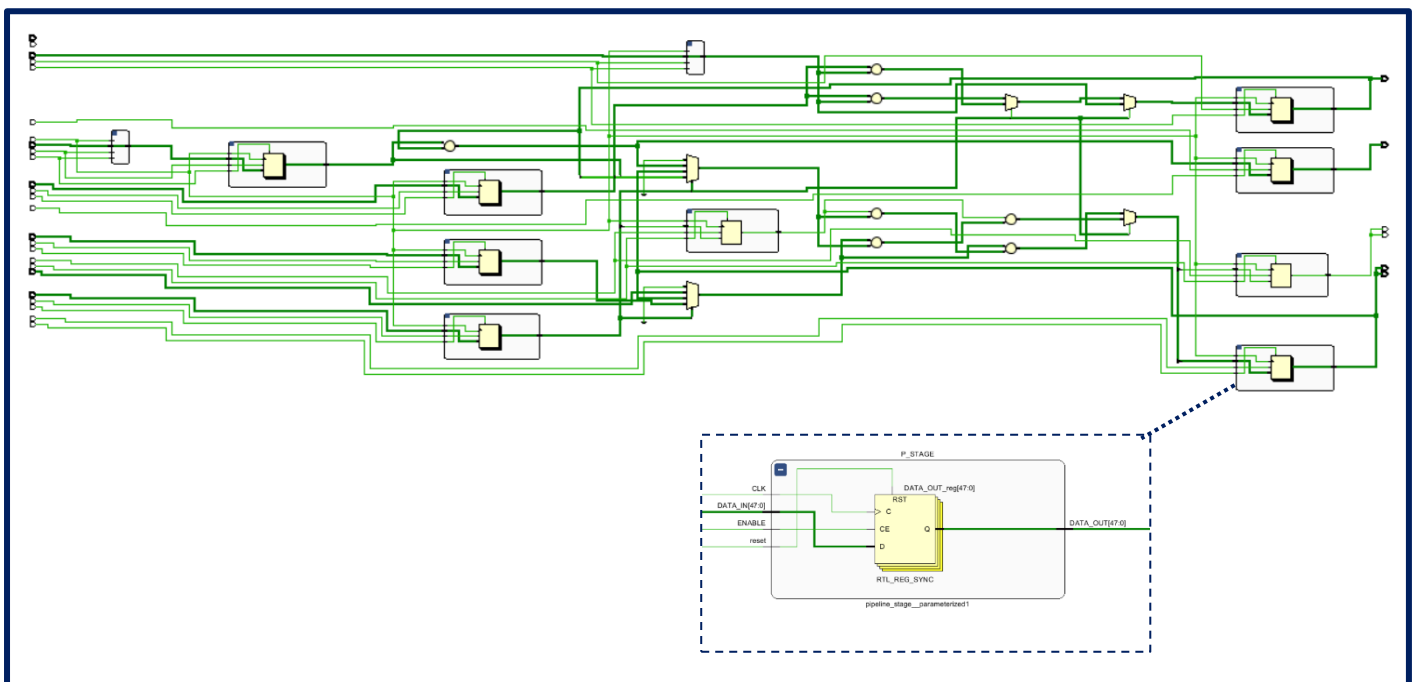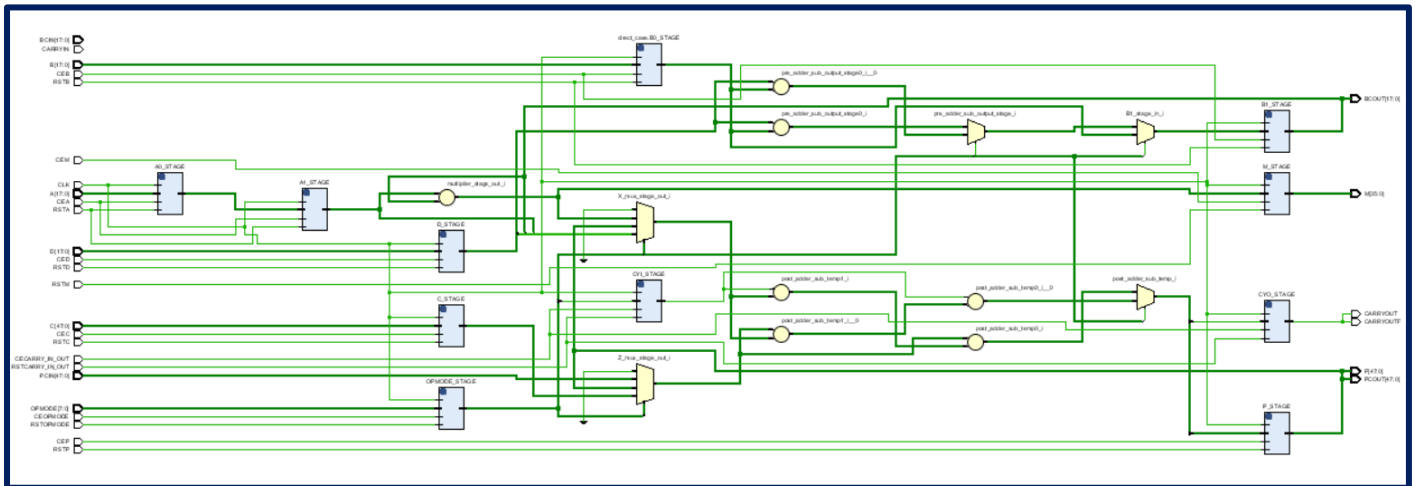


# 9.Synthesis

## 9.1. Messages tab

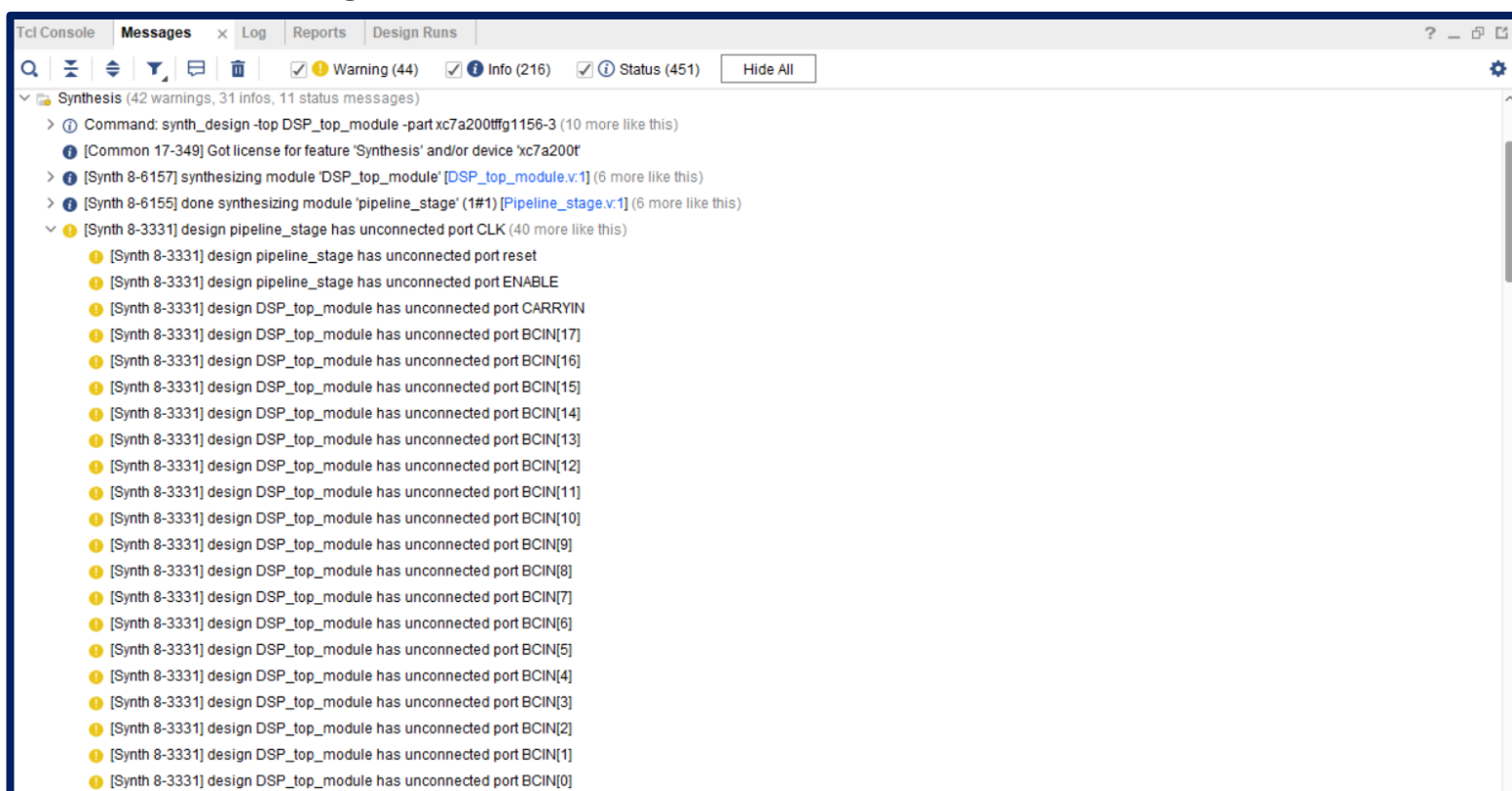

 
### 9.1.1. Comments on Warnings

At compile time, we can select whether a stage is to be registered or combinational. For stages designated as combinational, the Pipeline Stage functions as a direct connection between the input and output. This configuration results in other inputs, such as Enable and Clock, being left unconnected.



Regarding the warning about the B Cascaded Input (BCIN), this is because the port is not driven. This occurs as we have designed a single stage of the DSP48A1 slice and have not implemented cascading slices.

## 9.2. Netlist Generation

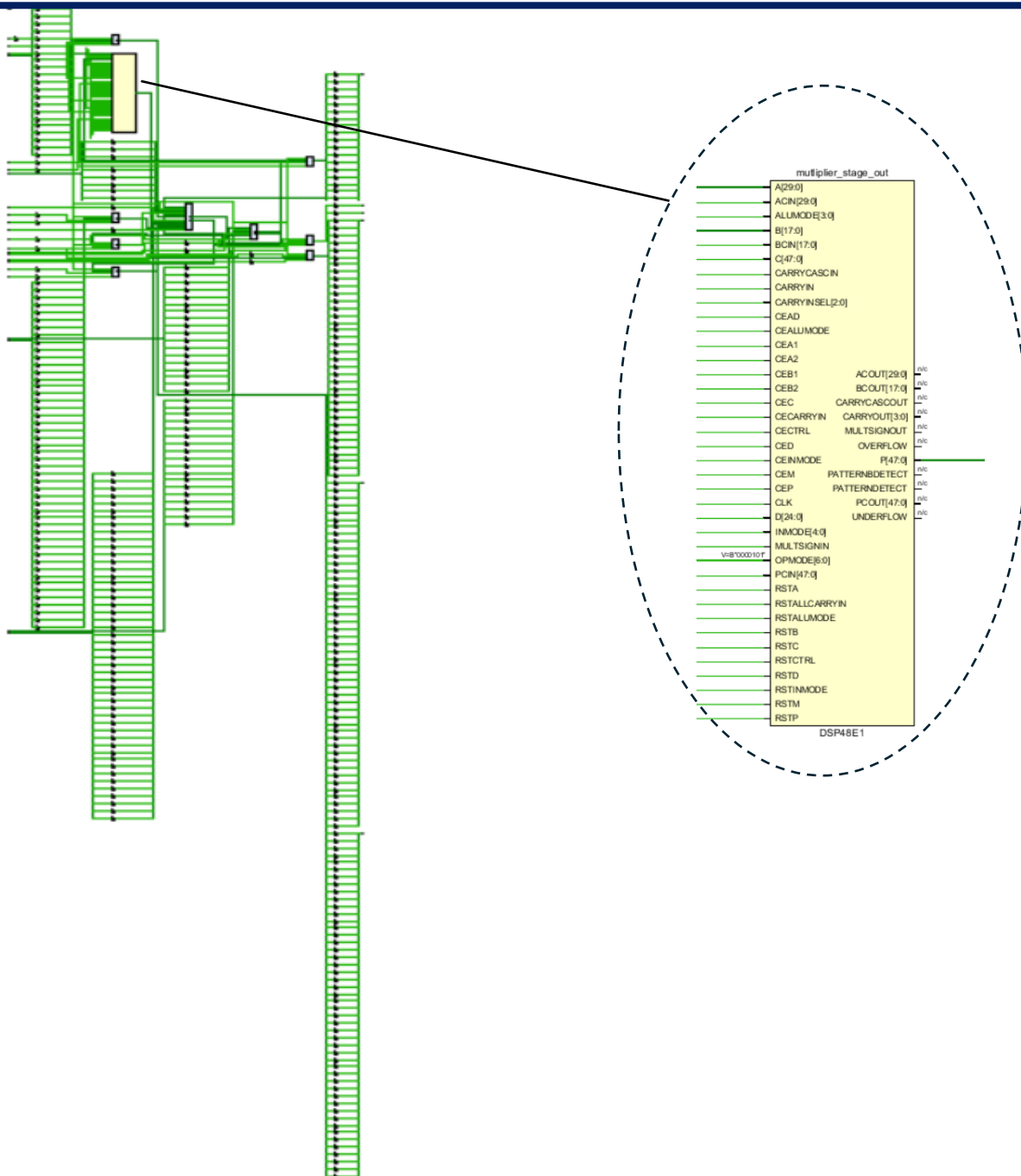

## 9.3. Report timing summary

Timing

Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 2.793 ns	Worst Hold Slack (WHS): 0.182 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 122	Total Number of Endpoints: 122	Total Number of Endpoints: 197

All user specified timing constraints are met.

## 9.4. Utilization Report


Timing					
Utilization					
Hierarchy					
Name	Slice LUTs (134600)	Slice Registers (269200)	DSPs (740)	Bonded IOB (500)	BUFCTRL (32)
DSP_top_module	230	196	1	327	1
A1_STAGE (pipeline_s...	0	18	0	0	0
B1_STAGE (pipeline_s...	0	18	0	0	0
C_STAGE (pipeline_st...	0	48	0	0	0
CYL_STAGE (pipeline_...	1	1	0	0	0
CYO_STAGE (pipeline...	0	1	0	0	0
D_STAGE (pipeline_st...	36	18	0	0	0
M_STAGE (pipeline_st...	0	36	0	0	0
OPMODE_STAGE (pip...	193	8	0	0	0
P_STAGE (pipeline_st...	0	48	0	0	0

# 10. Implementation

## 10.1. Message tab

Timing					
Utilization					
Tcl Console					
Messages					
Log					
Reports					
Design Runs					
Warning (44) Info (226) Status (456) Hide All					
Implementation (1 warning, 91 infos, 219 status messages)					
Design Initialization (11 infos, 7 status messages)					
Command: open_checkpoint (D:/My life/workshops/Digital Workshop IEEE/projects/DSP/Vivado/project_1/project_1.runs/impl_1/DSP_top_module.dcp) (6 more like this)					
[Netlist 29-17] Analyzing 207 Unisim elements for replacement					
[Netlist 29-28] Unisim Transformation completed in 0 CPU seconds					
[Project 1-479] Netlist was created with Vivado 2018.2					
[Device 21-403] Loading part xc7a200tfg1156-3					
[Project 1-570] Preparing netlist for logic optimization					
[Timing 38-478] Restoring timing data from binary archive.					
[Timing 38-479] Binary timing data restore complete.					
[Project 1-856] Restoring constraints from binary archive.					
[Project 1-853] Binary constraint restore complete.					
[Project 1-111] Unisim Transformation Summary: No Unisim elements were transformed.					
[Project 1-604] Checkpoint was created with Vivado v2018.2 (64-bit) build 2258646					
Opt Design (23 infos, 45 status messages)					
Place Design (23 infos, 90 status messages)					
Route Design (1 warning, 34 infos, 77 status messages)					
Command: route_design (76 more like this)					
[Common 17-349] Got license for feature 'Implementation' and/or device 'xc7a200t'					
DRC (1 warning)					
Pin Planning (1 warning)					
[DRC CFGBVS-7] CONFIG_VOLTAGE with Config Bank VCC0: The CONFIG_MODE property of current_design specifies a configuration mode (SPIx4) that uses pins in bank 14. I/O standards used in this bank have a voltage requirement of 1.80. However, the CONFIG_VOLTAGE for current_design is set to 3.3. Ensure that your configuration voltage is compatible with the I/O standards in banks used by your configuration mode. Refer to device configuration user guide for more information. Pins used by config mode: V28 (IO_L1P_T0_D00_MOSI_14), V29 (IO_L1N_T0_D01_DIN_14), V26 (IO_L2P_T0_D02_14), V27 (IO_L2N_T0_D03_14), W26 (IO_L3P_T0_DQS_PUDC_B_14), and Y27 (IO_L6P_T0_FCS_B_14)					
[Vivado_Tcl 4-198] DRC finished with 0 Errors, 1 Warnings					

## 10.2. Device

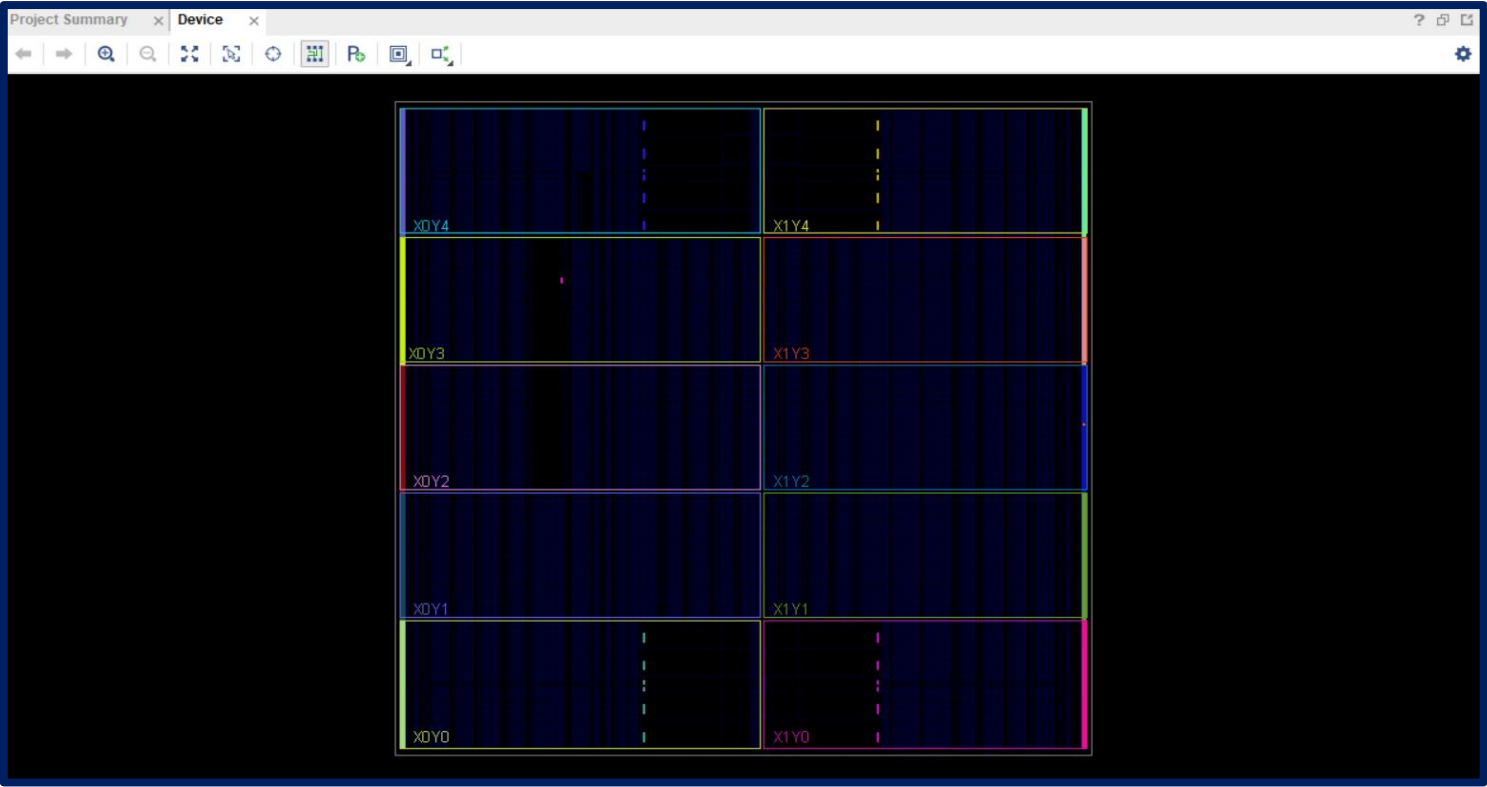

## 10.3. Design timing summary

Design Timing Summary		
Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 1.687 ns	Worst Hold Slack (WHS): 0.078 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 141	Total Number of Endpoints: 141	Total Number of Endpoints: 216
All user specified timing constraints are met.		

# 10.4. Utilization Report

## 10.4.1. Hierarchy

Tcl ConsoleMessagesTimingUtilization x ? \_ □ ▢

Q ⚙ % Hierarchy ⚙

Name	Slice LUTs (133800)	Slice Registers (267600)	Slice (33450)	LUT as Logic (133800)	LUT Flip Flop Pairs (133800)	DSPs (740)	Bonded IOB (500)	BUFGCTRL (32)
▼ DSP_top_module	230	215	106	230	50	1	327	1
A1_STAGE (pipeline_s...	0	18	8	0	0	0	0	0
B1_STAGE (pipeline_s...	0	36	8	0	0	0	0	0
C_STAGE (pipeline_st...	0	48	14	0	0	0	0	0
CY1_STAGE (pipeline_...	1	1	1	1	1	0	0	0
CY0_STAGE (pipeline...	0	2	2	0	0	0	0	0
D_STAGE (pipeline_st...	36	18	17	36	0	0	0	0
M_STAGE (pipeline_st...	0	36	13	0	0	0	0	0
OPMODE_STAGE (pip...	193	8	65	193	0	0	0	0
P_STAGE (pipeline_st...	0	48	12	0	0	0	0	0

## 10.4.2. Summary

